



Figure 2 Optional lowpass filters on the DACs' outputs remove switching artifacts from the sine and the cosine waveforms.