



Figure 1 The 200-MHz AD8130 differential-input line receiver/amplifier can serve as a basic building block in a high-frequency-capable current source.