



Figure 2 Adding an Analog Devices AD8065 buffer amplifier, IC₂, isolates the current-sampling resistor R_{SENSE} and reduces errors that IC₁'s input-bias current contributes.