



Figure 4 The complete circuit includes trimmer capacitor C_{COMP} , which compensates for stray capacitances in the circuit's packaged layout. Also, note wideband treatment of power-supply bypass capacitors.