



Figure 5 This circuit simulates switching-regulator output. You can independently set ripple amplitude, dc, frequency, and spike duration and height. A split-path scheme sums wideband spikes with dc and ripple, presenting the linear regulator with simulated switching-regulator output. A function generator sources waveforms to both paths.