



Figure 7 C_{IN} of $1\ \mu\text{F}$ and C_{OUT} of $10\ \mu\text{F}$ result in linear-regulator input (Trace A), output ripple (Trace B), and switching-spike content. Output spikes, driving $10\ \mu\text{F}$, have lower amplitude, but rise time remains fast.
