



**Figure 1** In a conventional switched-mode power supply's bootstrap circuit, trickle-charge resistor  $R_T$  and capacitor  $C_H$  supply start-up power to the pulse-width modulator and controller,  $IC_1$ .