



Figure 1 This USB-based GPIB controller requires only four ICs.