

AGC amplifier features 60-dB dynamic range

Julius Foit, Department of Microelectronics, CTU Prague, Czech Republic

When processing signals from analog sensors, you frequently encounter wide variations in attenuation among communication channels or sensors. Or, you face situations in which several identical sensors within a supervised system return signals of roughly similar spectral composition and dynamic range but with considerably different maximum amplitudes. Sometimes, it's possible to predict these and other variations and adjust the gain of preprocessing amplifiers. More frequently, you encounter unpredictable signals and thus lose data associated with nonrepeatable events. In these circumstances, an adaptive preamplifier with AGC (automatic gain control) can prevent measurement-channel saturation and data loss.

AGC preprocessing suppresses the absolute amplitude of a sensed signal while preserving the best possible resolution of individual spectral components' relative amplitudes. The circuit in this Design Idea offers one relatively simple and efficient approach to per-channel AGC. The circuit uses a method of direct low-level signal control using a short-circuited bipolar transistor. In **Figure 1**, a variable voltage divider comprising a fixed resistance, R_1 , and a variable resistance controls the signal's ac amplitude. The variable resistance comprises the differential resistance of a bipolar transistor, Q_1 , short-circuited

from base to collector. To vary Q_1 's resistance, you force direct current into the shorted transistor from a current source comprising voltage source V_{REG} and a high-value resistor, R_2 . To prevent R_2 from affecting the circuit's ac-voltage-transfer characteristic, R_2 's resistance must greatly exceed R_1 's.

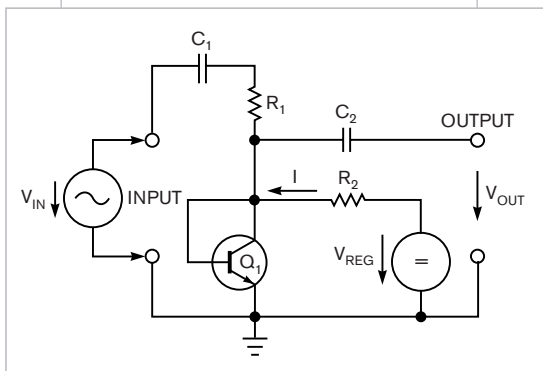


Figure 1 A short-circuited bipolar transistor forms one element of a basic attenuator circuit.

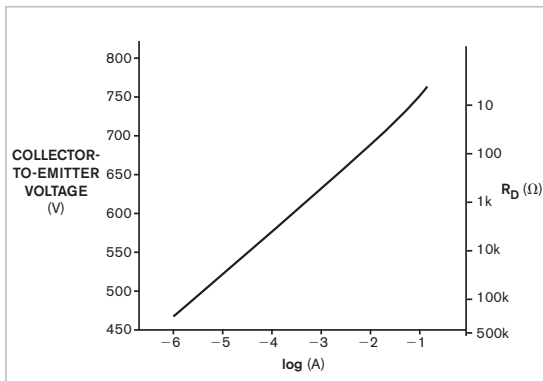


Figure 2 A VI characteristic shows the corresponding differential-resistance graph for a short-circuited BC337-16 transistor. (Note: The -16 denotes a sorted h_{FE} range of $100 < h_{FE} < 250$.)

DIs Inside

94 Precision active load operates as low as 2V.

96 Squeeze extra outputs from a pin-limited micro-controller.

For all reasonable values of positive current I —generally, less than the transistor's maximum rated emitter current (I_E)—transistor Q_1 's collector-to-emitter saturation voltage is less than its base-emitter threshold voltage, and the transistor operates in the active state. The shorted transistor's VI (voltage-versus-current) characteristic curve strongly resembles that of a PN diode and follows Shockley's Equation except for slightly higher dc-voltage values. That is, the device's voltage variation is proportional to the logarithm of the dc-current variation.

Therefore, the shorted transistor's differential resistance at every dc operating point along the VI curve is inversely proportional to the passing dc current; in other words, the device's differential conductance is directly proportional to the current. Because, in its active state, a common-emitter-connected bipolar transistor's current-amplification factor is typically 100 or more, the differential resistance accurately follows this rule over a broad range of currents.

Thus, varying V_{REG} in **Figure 1** varies the current, I , and controls the R_1 - Q_1 voltage-division ratio. Coupling capacitors C_1 and C_2 separate the

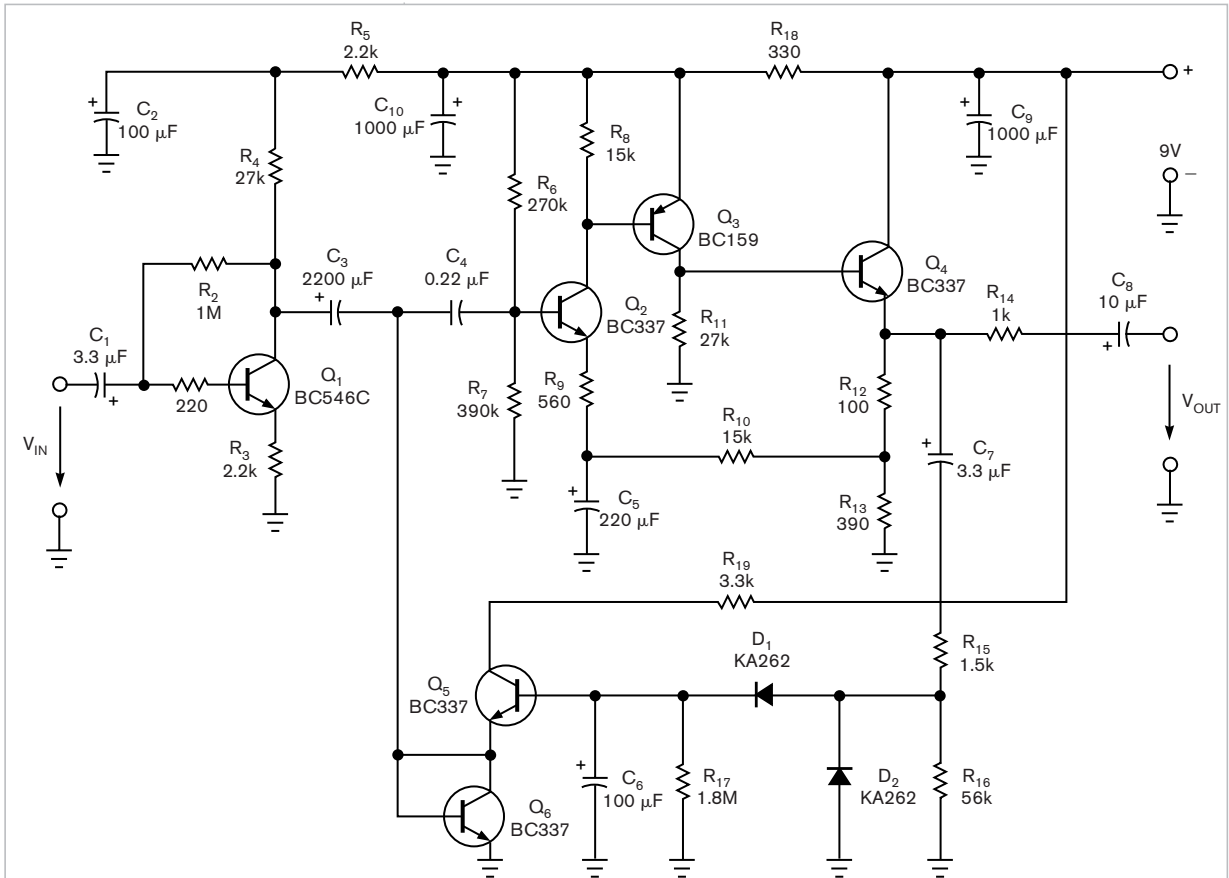


Figure 3 You can assemble this AGC circuit entirely from discrete components.

circuit's attenuator from the input-signal source and output load. **Figure 2** illustrates a typical small-signal bipolar transistor's short-circuited VI characteristic, showing that you can control differential resistance over at least five decades of range—that is, more than 100 dB.

In a practical circuit, the finite values of R_1 and R_2 limit the control range. For proper operation and to keep the signal's THD (total-harmonic-distortion) factor, k , below 5%, the output-voltage amplitude, V_{OUT} , should be just a few millivolts. Even with these limitations, this attenuator circuit appears to offer one of the best and simplest AGC circuits.

Figure 3 shows the completed circuit design. The input signal, V_{IN} , drives buffer stage Q_1 , whose unbypassed emitter resistor, R_3 , serves four purposes.

First, it increases Q_1 's differential output resistance to the approximate value shown in **Equation 1**:

$$R_{DI} \approx \frac{h_{11E} + h_{21E}R_3}{h_{11E}h_{22E}} \quad (1)$$

The increase in the circuit's differential output resistance is so large that the value of R_4 , 27 k Ω , almost exclusively determines the overall output resistance. Second, leaving R_3 unbypassed reduces Q_1 's voltage gain to:

$$A_{IC1} = (h_{22E}R_3 - h_{21E})R_4 / (R_3 + R_4)D_{hE} + [h_{21E} + 1 - h_{12E} + (R_3 + R_4)] R_3 + h_{11E} \approx -R_4 / R_3 \quad (2)$$

This equation simplifies to $A_{IC1} \approx R_4/R_3$. (Note that D_{hE} denotes the

determinant ($h_{11E} \times h_{22E} - h_{12E} \times h_{21E}$), which this Design Idea includes for theoretical accuracy. However, you can neglect the numerical value of D_{hE} for modern silicon transistors without significantly affecting the calculation's accuracy.) Third, as **Equation 2** shows, leaving R_3 unbypassed helps linearize the response of Q_1 's collector current-to-voltage drive. Fourth, Q_1 's differential base input resistance rises to: $R_{jBASE} = h_{11E} + h_{21E} \times R_3$, which is larger and less dependent on Q_1 's instantaneous operating point than h_{11E} alone.

In **Figure 3**, resistor R_4 forms the variable attenuator's fixed resistance, analogous to the upper resistor, R_1 , in **Figure 1**, and Q_6 forms the attenuator's variable-resistance element. Transistor Q_5 supplies Q_6 's collector-drive current, and Q_5 's common-emitter configura-
(continued on pg 92)

tion draws little base current. This approach enables use of a high value for AGC-release time-determining resistor R_{17} , thus permitting a long AGC-release time. Resistor R_{19} limits the maximum dc control current through Q_5 and Q_6 .

The large value of C_3 , when you compare it with Q_6 's minimum differential resistance—that is, its maximum signal amplitude—at full control, presents negligible reactance to the lowest frequency-signal-spectrum component. A voltage-doubler rectifier comprising D_1 and D_2 extracts a portion of the signal from output stage Q_4 and produces the control voltage for Q_5 . This arrangement accommodates both polarities of large peak amplitudes of nonsymmetrical signal waveforms. Resistor R_{15} determines the AGC's "attack" time. Too small values of R_{15} in combination with C_6 can lead to instability by creating a pole in the feedback-transfer function. Resistor R_{17} determines the AGC-release time.

To secure good response to high-frequency-signal components, use either Schottky or fast PN silicon diodes for D_1 and D_2 . The dc-coupled complementary cascade comprising Q_2 and Q_3 supplies most of the circuit's voltage gain. A 1-k Ω resistor, R_{14} , isolates Q_4 , the output-emitter follower, from the signal-output terminal. If necessary, you can use a lower resistance at R_{14} , but a large-capacitance connecting cable can provoke Q_4 into parasitic oscillation if R_{14} is too low.

Figure 4 shows the circuit's input-versus-output characteristics as measured with a sine-wave signal. The effective AGC range extends from 100- μ V- to 100-mV-rms input voltage, a 60-dB dynamic range. Output voltage varies less than 2 dB over this input range, reaching a nominal level of 775 mV rms at a -20-dB- (100- μ V-rms) input level. The input's 0-dB point is set arbitrarily at 1-mV-rms input, which corresponds to an 803-mV-rms output. The AGC attack time for a sinusoidal-input-signal step from 0 to 100 mV rms is approximately 0.3 sec, and the AGC

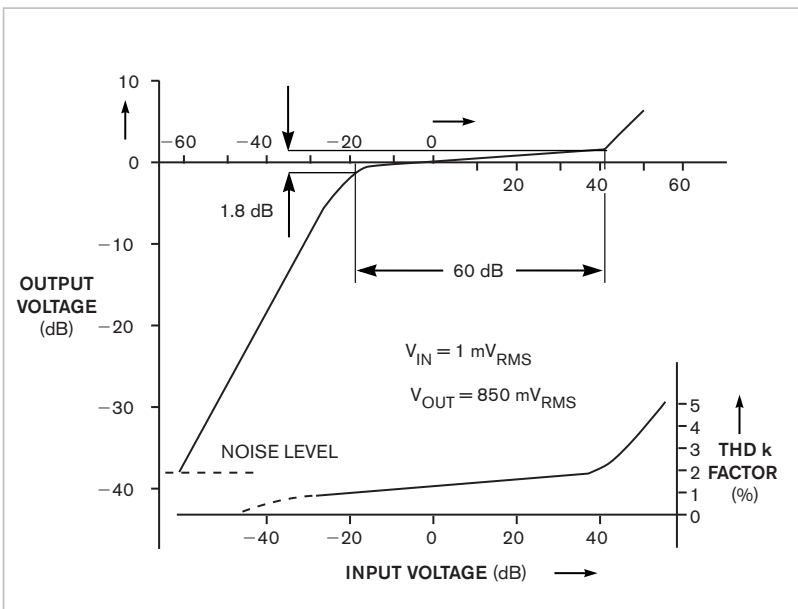


Figure 4 The circuit's input-versus-output characteristic shows a 60-dB control range (upper trace) and total harmonic distortion well below 5% over the control range (lower trace).



Figure 5 A single-sided pc board accommodates the assembled AGC amplifier.

release from 100-mV-rms input to -20 dB (100 μ V rms) is approximately 100 sec. **Figure 4** also includes a graph of THD versus input voltage. The distortion is well below a 5% THD limit throughout the input-voltage range.

To measure the attenuator's baseline input noise, terminate the input with its nominal 1-k Ω source resistance. At low input voltages, input stage Q_1 's noise limits the processed signal's usable dynamic range. The rms noise level is about -38 dB relative to the nominal output for input signals below the AGC

threshold. When the AGC becomes active, the SNR increases in proportion to the AGC reduction. For example, with a 0-dB- (1-mV-rms) input signal, the SNR increases to approximately 60-to-1.

If you assemble the circuit using the passive-component values in **Figure 3**, the amplifier's -3-dB bandwidth spans 45 Hz to 35 kHz. At a power-supply voltage of 9V, no-signal current consumption is approximately 12 mA. **Figure 5** shows a photograph of the assembled pc board. **EDN**

Precision active load operates as low as 2V

By Joel Setton, Crolles, France

This Design Idea presents a self-powered, precision-active-load circuit that improves on a previously published design (Reference 1). Added features include a wider operating-voltage range of 2 to 50V or higher and several flexible current-setting modes. The circuit in Figure 1 uses National Semiconductor's LM10, which suits this application. The LM10's reference section, IC_{1A}, generates a precision 1.2V reference voltage, V_S. Resistive divider R₁ and R₂ applies a fraction of V_S to IC_{1A}'s reference amplifier, which drives shunt regulator Q₁.

Transistor Q₃ acts as a current mirror of transistor Q₂'s collector current and supplies power to shunt regulator Q₁. Resistors R₉ and R₇ set the current-mirror ratio, and the current through resistor R₉ depends on the current through R₆, which V_S establishes. As a result, Q₃, which mirrors the collector current of Q₂, provides power to the shunt regulator. V_S sets R₆, which determines the current through R₉. Thus, the LM10's reference section regulates both its own power-supply voltage and the current that Q₃ provides.

At power-on, Q₂, Q₃, and Q₄ are all off. Resistor R₁₀ draws a small amount

of start-up current, which Q₃ amplifies to start the current-mirror process. When sufficient current flows through R₇, Q₄ saturates, and R₉ and R₇ then set the current-mirror ratio. The active load's power-handling section comprises the LM10's operational-amplifier section, IC_{1B}, and power transistors Q₆ and Q₈. A 10-turn precision potentiometer, P₁, and range-selection switch, S₁, set the load current as follows:

On Range A, the load current varies at 1A per turn of P₁—that is, 10A maximum with P₁ set fully clockwise. On Range B, the load current varies at 100 mA per turn of P₁—that is, 1A maximum with P₁ set fully clockwise. On Range C, an external voltage source that connects to R₁₃ controls the load current at a rate of 1A per volt with P₁ set fully clockwise. You can drive the external input with a function generator to test a power supply's transient response. On Range D, the load circuit emulates an adjustable power resistor with load current proportional to the voltage across the load's terminals. The equivalent resistance varies with P₁'s setting—that is, $R_{LOAD} = 100\Omega/N_{TURNS}$. Range E is similar to D, with a resistance of $10\Omega/N_{TURNS}$.

To calibrate the circuit, connect it to a suitable power supply delivering any voltage from 2 to 50V. First, set P₁ to one turn—that is, one-tenth of full-scale—and S₁ to Range B. Adjust R₁₇ for a 100-mA output current. Then, rotate P₁ fully clockwise and adjust R₂₀ to set the output current to 1A. Repeat these two adjustments in sequence because they interact slightly. Current that IC₁ draws through Q₃ sets the minimum current through the load circuit at slightly less than 1 mA.

Because the circuit operates at 2 to 50V, it is suitable for testing the low-voltage outputs of a PC's power supply. You can extend the maximum voltage by selecting suitable transistors for Q₂, Q₃, and Q₅ through Q₈; the LM10's regulated power-supply voltage does not link to the external voltage. Note that when dissipating large amounts of power, transistors Q₆ and Q₈ require adequate cooling to maintain safe junction temperatures. EDN

REFERENCE

1 Toffoli, Tommaso, "Self-powered dummy load checks out multiple power supplies," *Electronic Design*, April 17, 2000, pg 118.

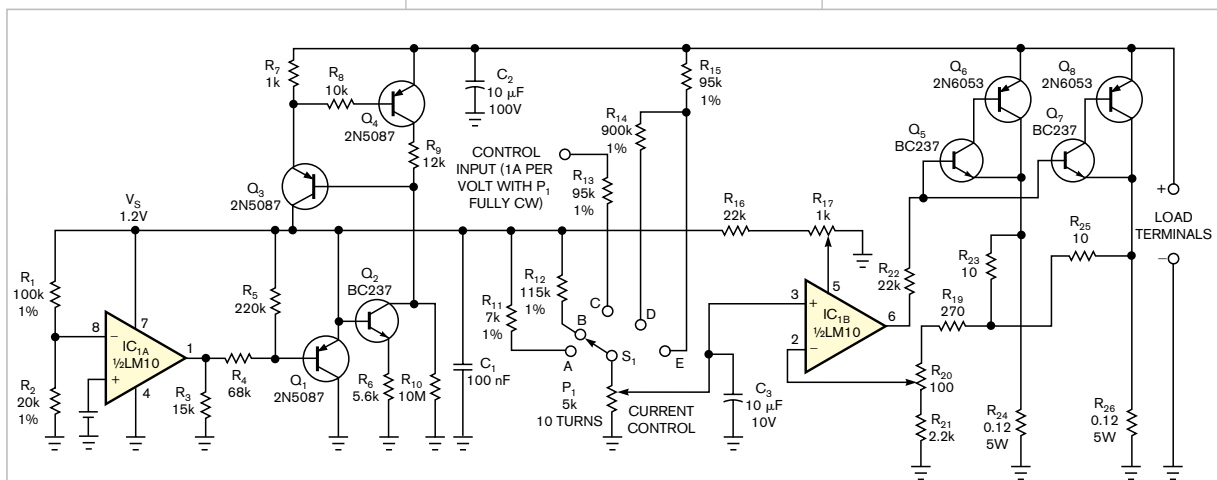


Figure 1 This versatile precision load circuit draws constant current or emulates an adjustable power resistor.

Squeeze extra outputs from a pin-limited microcontroller

Abel Raynus, Armatron International Inc, Malden, MA

Many of today's designs use low-cost microcontrollers from Freescale and Microchip, but during the last decade, device packages have resorted to ever-smaller footprints featuring as few as eight or even six pins. Although these packages minimize pc-board area, they also reduce the number of available I/O pins and pose problems for designers who need to add one more function without migrating to a device that occupies a larger package.

To overcome a shortage of inputs, a designer can increase a small microcontroller's inputs by writing a program

that multiplexes and polls the input pins. However, this approach doesn't lend itself to extending outputs, because most designs require simultaneously driving multiple pins. **Figure 1** shows how to solve the problem by adding a shift register.

For example, you can add an eight-LED bar graph to a design based on IC₁, Freescale Semiconductor's 9-bit, flash-memory MC68HC908QT1 microcontroller, which has only eight pins. The device includes only four general-purpose outputs and thus by default cannot drive eight discrete LEDs. To solve

the problem, you can add IC₂, a 74HC595 serial-input/serial-output/parallel-output latching shift register available from On Semiconductor and other vendors. The register's latching function allows selective drive of only those LEDs associated with specific data bits.

According to its data sheet, the 74HC595 accepts signals through the SPI protocol. Unfortunately, low-end microcontrollers, such as the MC68HC908QT1, lack SPI hardware, but you can simulate the SPI in software by following these steps:

1. Unlatch the shift register's outputs by deasserting microprocessor IC₁'s PA4 pin.
2. Starting with the MSB, copy a bit from the processor's internal data register and transfer the bit to the processor's PA0 (SD) output.
3. Generate a clock pulse at Pin PA1.
4. Repeat steps 2 and 3 for all eight data bits.
5. Assert the microprocessor's PA4 output to latch the data into IC₂, the 74HC595.

Figure 2 shows the timing diagram for transmitting data byte \$F0 from IC₁ to IC₂.

Available from the online version of this Design Idea at www.edn.com/050804di1, **Listing 1** illuminates the LEDs by sending five consecutive bytes to IC₂ and the LEDs: \$03, \$0c, \$30, \$c0, and \$55. The first four bytes progressively illuminate two LEDs along the bar-graph display at one step per second. The last byte illuminates and latches all odd-numbered LEDs. The **listing** contains only commonly used instructions that easily translate into other microcontrollers' assembly languages.

The SPI requires only three output pins, which frees the microcontroller's remaining I/O pins for other functions and allows remote installation of the shift register/LED driver—for example, on a separate display board with the LEDs. Also, when suitably buffered, the register's outputs can drive other loads, such as motors, relays, and incandescent lamps. **EDN**

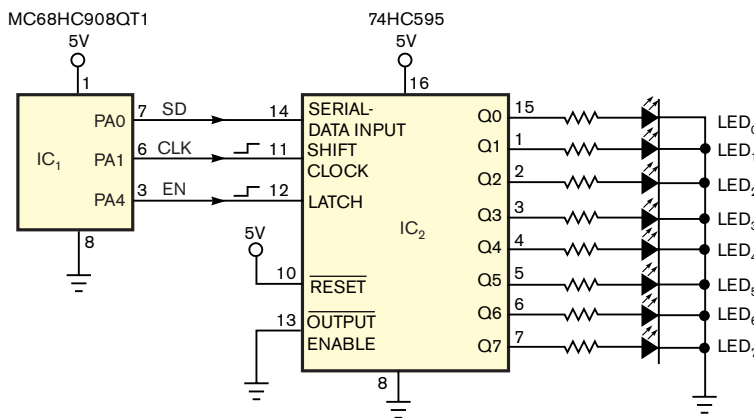


Figure 1 Do you need more outputs? You can emulate an SPI in software to add a shift register to a pin-limited microcontroller.

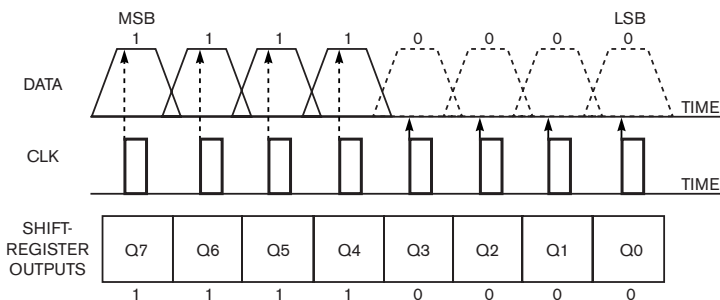


Figure 2 The sample timing diagram illustrates the loading of \$F0 byte into an external shift register.