



Figure 1 A short-circuited bipolar transistor forms one element of a basic attenuator circuit.