



Figure 2 Cascaded dual integrators implement a quadrature sine-wave oscillator, with blocks 3 and 4 forming a low-pass filter. Again, the circuit design uses no external components. The values shown are for a 27.2-kHz oscillator.