



Figure 1 This current sensor uses a variable-frequency oscillator, Q<sub>1</sub>, and a PLL, IC<sub>1</sub>, to measure current in an isolated circuit.