



Figure 1 A small-signal transistor, Q<sub>2</sub>, provides an output-current limit for this emitter-follower power amplifier.