



Figure 2 Substituting a shunt regulator, IC₁, for Q₂ in Figure 1 improves the output-current-limit accuracy.