



Figure 1 In a typical application, fan-controller IC₁ and transistor Q_A apply pulse-width-modulated current to vary a fan's speed as a function of temperature.