



Figure 3 Output voltage at Q_2 's collector shows a linear relationship versus the controller's pulse-width-modulated output-duty cycle. (The pulse width increases as the temperature increases.) The fan's operating voltage corresponds to the difference between Q_2 's output voltage and the 12V supply rail.