



Figure 2 The principal difference between this current-mode regulator and the voltage-mode circuit is in the source of the modulating ramp. In this circuit, the ramp voltage is proportional to the buck-switch voltage.