



**Figure 3** The three main current waveforms in a buck regulator are the buck-switch current, the free-wheel-diode current, and the inductor current. The buck-switch and the diode currents sum to form the inductor current.

---