



Figure 4 This practical controller overcomes current-mode regulators' noise susceptibility by emulating the buck-switch-current signal and using the emulated signal for current-mode control.