

# Signal conditioning for high-impedance sensors

MAINTAINING ACCURACY IN CIRCUITS THAT PROCESS SIGNALS FROM HIGH-IMPEDANCE SENSORS PRESENTS UNIQUE CHALLENGES. FIRST, YOU NEED TO IDENTIFY WHEN TO USE SPECIAL DESIGN TECHNIQUES. THEN, YOU MUST CHOOSE DEVICES THAT BUFFER AND PROTECT THE SENSORS AND CIRCUITS WITHOUT DESTROYING THEIR ACCURACY.

If you had the option, you probably wouldn't use high-Z (high-impedance) sensors. Their sensitivity to external noise, solder-flux residue, particle tracking, bias currents, and distant charges can make repeatable measurements difficult. High-Z sensors have an upside, though: They don't self-load, and they inherently use little power. For certain variables, such as pH, light, acceleration, and humidity, the most practical sensors are high-Z devices. Because nature offers them, expediency urges their use. Careful attention to design can minimize the devices' tendency to receive adverse effects from the world around them. As an interesting note, with the advent of practical superconduction, impedance values have achieved an infinite range.

When you make measurements to characterize the behavior of any circuit that processes signals from high-Z sensors, you should drive the circuit's inputs through a high Z or a high resist-

ance. Every engineer who works with signal conditioners for high-Z sensors should have some high-value reference resistors at hand. Vishay ([www.vishay.com](http://www.vishay.com)) offers surface-mount resistors with values to 50 GΩ. Samples with values of 1 and 2 GΩ were available off the shelf at press time. The Mini-Mox series from Ohmite ([www.ohmite.com](http://www.ohmite.com)) contains leaded 10- and 100-GΩ resistors. All of these high-value resistors are remarkably "stiff" (conductive, nonisolating). For example, a colleague warns users not to touch the resistor bodies, lest skin-oil deposits reduce the impedance.

This warning suggested an experiment. Connecting a Keithley ([www.keithley.com](http://www.keithley.com)) Model 614 electrometer across the resistor leads resulted in a meter reading of 9.9 to 10 GΩ. After thoroughly touching and squeezing the resistor body from lead to lead with oily fingers and then backing away, the meter returned to precisely where it had been: 9.9 to 10 GΩ. This test shows only that skin oils are not an immediate threat to these resistors. To ensure reliability over time and humidity, sound laboratory practice still exhorts keeping components, pc boards, and insulators clean. Skin-oil conductivity is known to vary among individuals. For cleaning, Ohmite recommends using isopropyl alcohol and lint-free wipes and baking the device at 75°C for one hour to drive off moisture. When performing an impedance measurement of this type, bear in mind that the insulator in the cable is entirely in parallel with the resistor under test. Limiting error to 1% in a 100-GΩ-resistor measurement requires an overall insulator impedance of no less than 10 TΩ. The only way around this limitation is to perform an open-circuit calibration to measure and mathematically remove any shunt resistance. The Keithley 614 lacks this feature, but it still performs well, reinforcing the idea that, compared with an insulator, a 10-GΩ resistor is indeed relatively stiff.

## ENEMIES OF HIGH-Z CIRCUITS

When Z is high, leakages, current noise, bias currents, and static voltages dominate the errors, so dealing with high-Z circuits means minimizing those quantities. The most common and addressable form of leakage is solder-flux residue. Carefully clean any board that supports high-Z circuits to remove all flux. Washers that board manufacturers use can be contaminated. Space traces beyond the minimum design rules to the extent that board area allows. For insulators, FR-4 usually causes no problem,

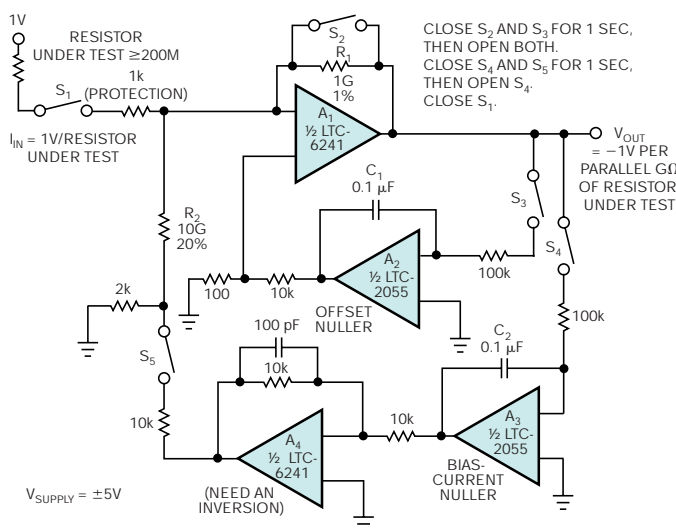


Figure 1 Using nulling techniques is tempting, and you can sometimes make them work with much effort and shielding. But making a "perfect" amplifier like this one becomes expensive and departs from the high reliability of solid-state design. You may be bankrupt before your design reaches production.




The circuit in **Figure 1** incorporates two force-balance nulling techniques. To follow the operation, assume that all the switches are open and then close  $S_2$  and  $S_3$ , thereby engaging ultra-precision integrating amplifier  $A_2$  and forcing  $A_1$ 's output to ground.  $A_1$ 's input offset appears at its positive input, and  $C_1$  stores 101 times this offset. Opening  $S_3$  allows  $A_1$  to function normally again, but with 1 mV of effective offset and approximately 1 mV/sec of drift. Now, opening  $S_2$  puts feedback resistor  $R_1$  in the circuit and causes an output voltage equal to  $I_{BIAS} \times R_1$ —typically, 1 mV. Closing  $S_4$  and  $S_5$  nulls  $A_1$ 's output again, but this time through  $A_3$ .  $A_1$ 's bias current now goes through  $R_2$ , and  $C_2$  stores it as a voltage at 60 mV/pA. Opening  $S_4$  ends the nulling phase.

Closing  $S_1$  connects the input drive—the resistor under test—and a voltage source. Although the amplifier is now nearly perfect, it doesn't remain so for long. Drift on capacitors  $C_1$  and  $C_2$  requires a new nulling phase within several seconds; otherwise, the amplifier's specifications may degrade beyond those of an unaided LTC6241. **Figure 2** shows a simpler method. Rather than trying to perfect the amplifier, this circuit instead chops the excitation to allow subtraction of the amplifier contributions. Also, the resistor under test is now in the feedback path, so the output is proportional to the resistor's resistance rather than its admittance. Rise time is 10 msec (10 to 90%) with a 1-G $\Omega$  resistor, so the excitation should be no faster than about 10 Hz to ensure adequate settling.


## PROTECTING A HIGH-IMPEDANCE CIRCUIT

How can you protect a high-Z circuit without affecting its input impedance? Strictly speaking, you can't, but you can come close. One of the best ways is to use a series resistor and some series inductance, even if it's just a length of trace. The inductance and parasitic elements spread out an ESD (electrostatic-discharge) pulse and improve the odds that it will jump to a chassis before it gets to anything sensitive. You can further improve those odds by introducing a spark gap in the layout near the connector pin to be struck. This approach is cheap and effective, but it can cause problems in higher density digital designs. The spark gap re-emits a strong EMI (electromagnetic-interference) wave, including some eerie blue. This phenomenon repeatedly crashed an onboard but distant 486 microprocessor, fortunately without harming the hardware. The protection you require depends on the level of immunity you specify for the design. In this case, the spark gap is a failure, because designers did not allow for PC-reset interventions. For analog designs or simple digital designs, spark gaps should not be a problem. Gas-discharge tubes, which are also available as components, are other alternatives.

Almost anything you do with diode clamps can cause leakage. Schottky diodes are probably out of the question because they tend to leak more. Ultralow-leakage diodes include the CMPD6001 series from Central Semiconductor ([www.centralsemi.com](http://www.centralsemi.com)) and the BAS416 from Philips. But the maximum-leakage specification, even when devices are cold, is 500 pA to 5 nA. The high-temperature specifications are even worse, often running into microamps. For the lowest leakage performance, JFET junctions still outperform diodes. The 2N4393, available from Vishay in an SOT-23 package, typically leaks 5 pA at room

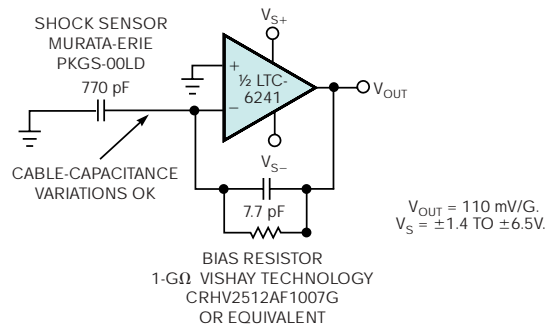

**Figure 4** In this classic inverting-charge amplifier, variations in cable capacitance—that is, length—do not affect the signal gain. Use this circuit when the accelerometer is remote from the amplifier and the cable length is unspecified. Drawbacks are that the low-valued feedback capacitor sets the gain, and the bias resistor working into the same feedback capacitor determines the low-frequency performance.

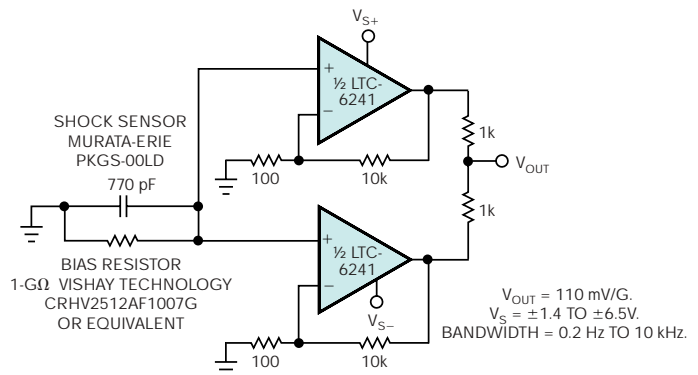

**Figure 5** This noninverting-charge amplifier offers two advantages: You can connect stages in parallel to reduce voltage noise, and the bias resistor works into higher capacitance for better low-frequency response.

temperature and 3 nA at 100°C (**Figure 3**). Compare this leakage with the maximum-specified bias current of 75 pA at 70°C for the LTC6241. Adding even good diodes can cause a significant degradation. Some design work can help offset this problem, however. For example, consider the tracking-limiter circuit (**Figure 3**).  $A_2$  back-biases the diodes, and  $C_1$  stores the average dc voltage. The system shunts overvoltages and spikes to the reservoir capacitor but allows dc through with unity gain, protecting the inputs and improving input-overload-recovery time. For dc gain, simply short  $C_1$  and move the input from  $A_2$  to  $A_1$ 's inverting input; inverting circuits are easier to protect, because you can simply connect the diodes to ground.

## HOW HIGHER Z HELPS

**Figures 4** and **5** show two approaches to amplifying signals from a capacitive sensor. The sensor in both cases is a 770-pF piezoelectric shock-sensor accelerometer, which generates charge under physical acceleration. **Figure 4** shows the classic charge-amplifier approach. The op amp is in the inverting configuration, so the sensor looks into a virtual ground. The op-amp action forces all of the charge the sensor generates

across the feedback capacitor. Because the feedback capacitance is 0.01 times the sensor capacitance, the voltage across the feedback capacitor is 100 times what would have been the sensor's open-circuit voltage. So, the circuit gain is 100. The benefit of this approach is that the circuit's signal gain is independent of any cable capacitance between the sensor and the amplifier. Hence, designers favor this circuit for remote accelerometers whose cable length may vary. Difficulties with the circuit are inaccuracy of the gain setting with the small capacitor and low-frequency cutoff because the bias resistor works into the small feedback capacitor.

**Figure 5** shows a noninverting-amplifier approach. This approach has many advantages. First, resistors, rather than a small capacitor, accurately set the gain. Second, the low-frequency response improves because the bias resistor working into the large 770-pF sensor, rather than into a small feedback capacitor, dictates the cutoff frequency. Third, you can sum and make parallel the noninverting topology for scalable reductions in voltage noise. This circuit's only drawback is that the parasitic capacitance at the input slightly reduces the gain. This circuit is a good fit for applications in which parasitic input capacitances, such as traces and cables, are relatively small and invariant.

When you calculate the bias resistance for the desired low-frequency cutoff, consider that you may want to make the bias resistor's value still larger. Doing so reduces the noise floor at low frequencies. For example, if you want to support frequencies as low as 10 Hz at  $-3$  dB, the bias resistor works out to

**MORE AT EDN.COM** ▶

Go to [www.edn.com/ms4177](http://www.edn.com/ms4177) and click on Feedback Loop to post a comment on this article.

$1/2\pi \times 10 \text{ Hz} \times 770 \text{ pF} = 20 \text{ M}\Omega$ . At 10 Hz, the 20-M $\Omega$  resistor contributes 580 nV/ $\sqrt{\text{Hz}}$  of noise, which is 3 dB down, just like the signal. If you make the resistor value 1 G $\Omega$ , the accelerometer capacitance effectively attenuates the resistor's 4000-nV/ $\sqrt{\text{Hz}}$  noise to 80 nV/ $\sqrt{\text{Hz}}$ , but the signal is barely attenuated. Sometimes, impedance higher than that normally required actually helps.

Devices and materials are available to support and protect high impedances. Dealing with high impedance requires a knowledge of what are otherwise minuscule phenomena. Sometimes, quantization of phenomena such as current noise can be challenging, but with the right circuit techniques, measurements become meaningful and repeatable. A proper breakdown of error sources, such as leakage, settling time, voltage noise, and current noise, helps the circuit designer to know what to expect. **EDN**

---

#### ACKNOWLEDGMENT

*The author acknowledges the contribution of Peter Haak for his input on gain calibration during current-noise measurements in transimpedance circuits.*

---

#### AUTHOR'S BIOGRAPHY

*Glen Brisebois is an applications engineer responsible for customer support for op amps, comparators, references, and rms-to-dc converters at Linear Technology Corp (Milpitas, CA). He holds bachelor's degrees in physics and electrical engineering from the University of Alberta (Edmonton, AB, Canada).*

---