



Figure 2 You can more easily achieve similar accuracy with chopped-excitation techniques. The amplifier's characteristics are not enhanced but rather measured and subtracted. What are the op amp's offset and bias current? It doesn't matter much.
