



Figure 3 The tracking clamp has protection diodes, but A_2 back-drives them to the same voltage as the input. The zener diode and its capacitor carry most of the clamp current. R_1 and R_2 keep current away from the amplifiers.