



Figure 4 In this classic inverting-charge amplifier, variations in cable capacitance—that is, length—do not affect the signal gain. Use this circuit when the accelerometer is remote from the amplifier and the cable length is unspecified. Drawbacks are that the low-valued feedback capacitor sets the gain, and the bias resistor working into the same feedback capacitor determines the low-frequency performance.