



Figure 5 This noninverting-charge amplifier offers two advantages: You can connect stages in parallel to reduce voltage noise, and the bias resistor works into higher capacitance for better low-frequency response.