



**Figure E** This high-frequency current-noise-measurement circuit emulates a photodiode transimpedance amplifier in which  $C_2$  replaces the photodiode.  $R_1$  and  $C_1$  enable high-frequency gain calibration.  $C_1$  is a parallel combination to minimize parasitic inductance.