



Figure 1 This compendium of constant-current circuits includes current sinks (a, b, and c), a bipolar sink or source (d), and a current source (e).