

Op amp can source or sink current

Alfredo H Saab and Steve Logan,
Maxim Integrated Products Inc, Sunnyvale, CA

When you design for electronics applications, such as sensor or amplifier bias supplies or special waveform generators, a controlled constant-current source or sink circuit can serve as a useful building block. These circuits exhibit high dynamic-output impedance and deliver relatively large currents within an allowed range of compliance voltage. You can implement a constant-current circuit with an op amp and a discrete external transistor, but you can also design a bipolar version of a current source or sink around a single op amp and a few resistors (Figure 1). The constant-current sink circuits in Figure 1a through Figure 1c offer various compromises between precision, dynamic impedance, and compliance range.

The circuit in Figure 1d describes a bipolar current source with a simpler feedback configuration than that of the usual Howland-current pump, which requires positive feedback and presents variable input impedance. Figure 1e shows a constant-current source. All of these circuits exhibit excellent linearity of output current with respect to input voltage.

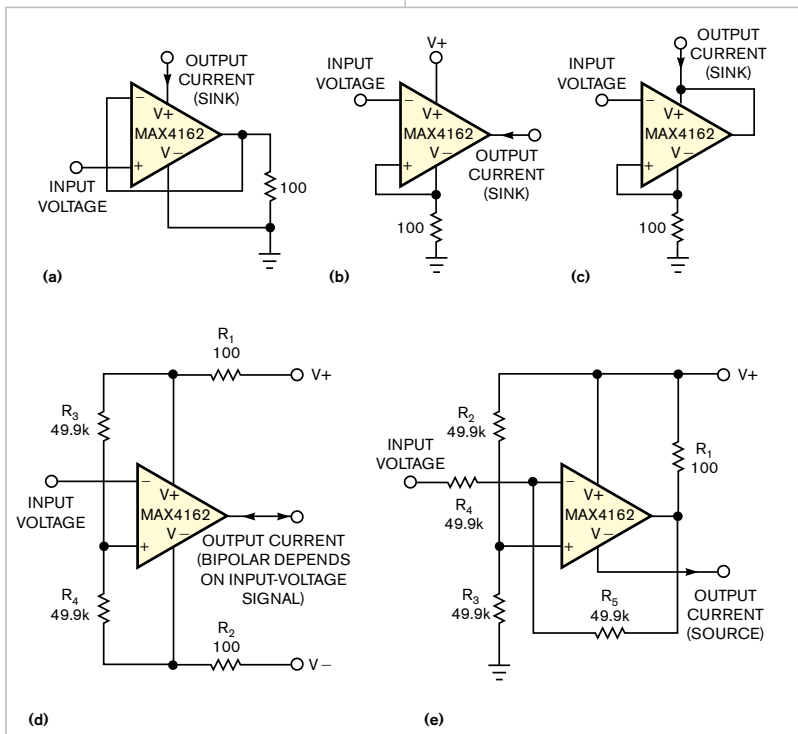


Figure 1 This compendium of constant-current circuits includes current sinks (a, b, and c), a bipolar sink or source (d), and a current source (e).

DIs Inside

76 Simple digital filter cleans up noisy data

78 Single switch selects one of three signals

80 Low-cost audio filter suppresses noise and hum

82 Microprocessor's single-interrupt input processes multiple external interrupts

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

The output from the circuit in Figure 1a includes an uncertainty due to the op amp's quiescent current, which adds to the calculated output current. For example, in most applications, you can neglect the MAX4162 op amp's quiescent current of approximately 25 μ A. The circuit in Figure 1b behaves similarly, but its quiescent current subtracts from the ideal output-current value. The circuit in Figure 1c provides a current sink with no quiescent-current error, and the circuit in Figure 1d presents a bipolar output—that is, it sinks or sources current—depending on the polarity of the input voltage. Its performance depends on close matching for the resistor pairs R_1 and R_2 and R_3 and R_4 and good tracking of the positive- and negative-power-supply voltages. Any difference between the absolute values of the supply voltages appears as an offset current at 0V input voltage. To achieve insensitivity to power-supply-voltage variations, the current-source circuit in Figure 1e requires close matching of resistor pairs R_2 and R_3 and R_4 and R_5 .

You can use the following equations to calculate output currents for the cir-

cuits in **Figure 1**. Note that $R_{LOAD} = 100\Omega$ in these examples. In **Figure 1a**, $I_{OUT} = -V_{IN}/R_{LOAD} + 25\ \mu A$; in **Figure 1b**, $I_{OUT} = -V_{IN}/R_{LOAD} - 25\ \mu A$; in **Figure 1c**, $I_{OUT} = -V_{IN}/R_{LOAD}$; in **Figure 1d**, $I_{OUT} = -2 \times V_{IN}/R_{LOAD}$; and, in **Figure 1e**, $I_{OUT} = V_{IN}/R_{LOAD}$. The equation for circuit **1d** assumes perfect match-

es—that is, $R_3 = R_4$, $R_1 = R_2$, and $V+ = V-$. It also assumes that R_4 is much greater than R_1 .

For a fixed value of output current in each of the five circuits in **Figure 1**, the graphs of **Figure 2** show the circuits' dynamic impedance and range of useful output voltage (current compli-

ance). The graphs show a high nominal output current of 5 mA to better display the higher end of the current-amplitude range. Depending on your application, you can optimize each circuit's dynamic impedance and current range through a judicious choice of op amps and resistor values.**EDN**

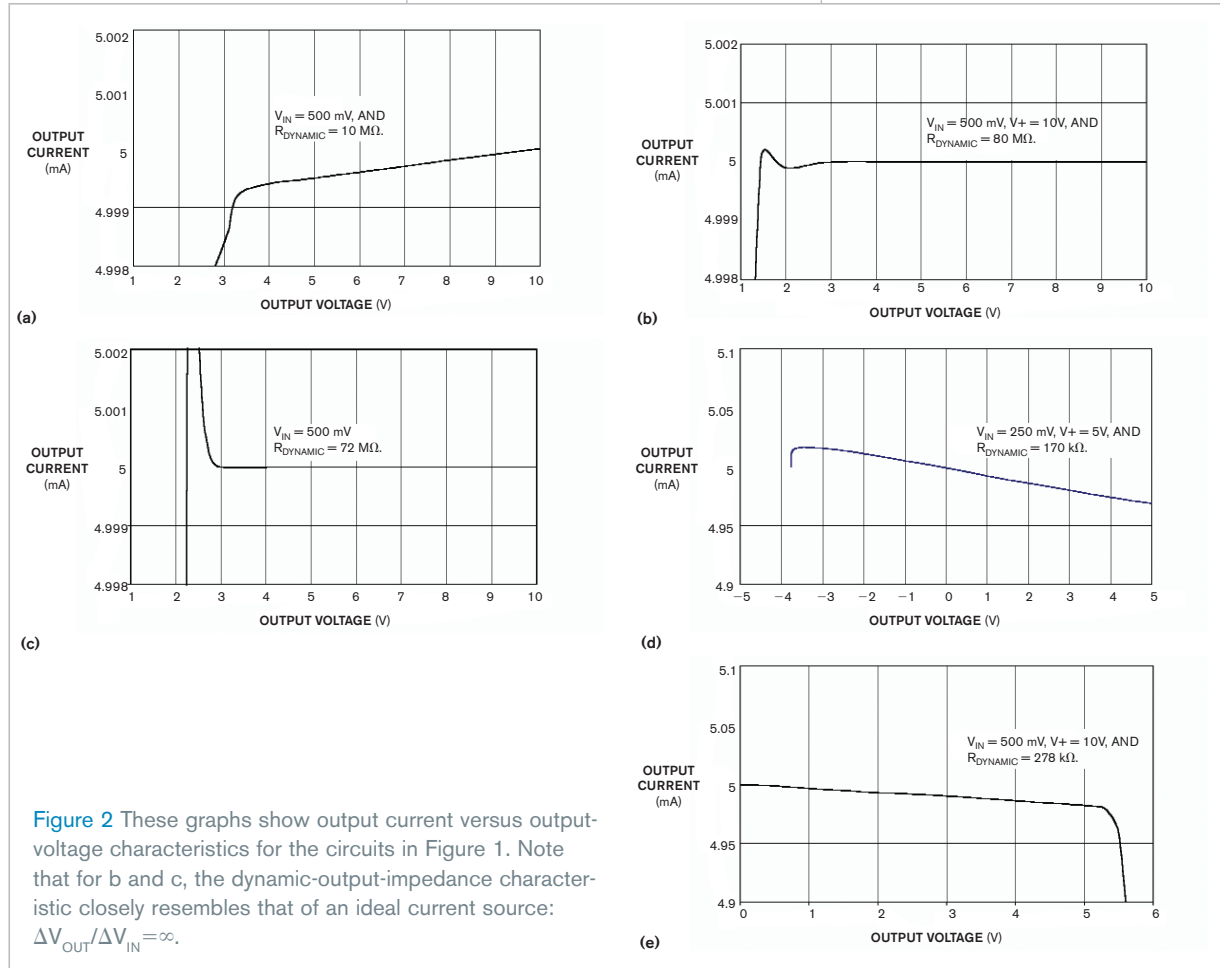


Figure 2 These graphs show output current versus output-voltage characteristics for the circuits in **Figure 1**. Note that for **b** and **c**, the dynamic-output-impedance characteristic closely resembles that of an ideal current source: $\Delta V_{OUT}/\Delta V_{IN} = \infty$.

Simple digital filter cleans up noisy data

Richard Rice, Oconomowoc, WI

Many systems use an ADC to sample analog data that temperature and pressure sensors produce. Sometimes, system noise or other fac-

tors cause the otherwise slowly fluctuating data to “jump around.” To reduce higher frequency noise, designers often install an analog RC (resistor-capaci-

tor) lowpass filter between the sensor and the analog-to-digital-conversion stage. However, this approach is not always ideal or practical. For example, a long time constant of minutes would require very large values for R and C .

Figure 1 shows an analog RC lowpass filter and its design equations. As an alternative, you can clean up noisy signals that remain within the ADC's lin-

selected output does not change, making the circuit a good choice for applications requiring nonvolatile operation. Quiescent-current consumption averages only about 15 μA at room temperature, 25°C, a low value even for battery-powered applications.

The heart of the circuit comprises a dual JK flip-flop, IC₃, that's configured as a 2-bit ripple counter. Without additional circuitry, the counter would allow selection of four signal sources. Upon initial application of power, a reset circuit comprising R₁, C₁, and IC_{1B} always sets the CH₁ output to a logic-low level.

When the \bar{Q} outputs of IC₃, pins 2 and 14, both go to logic zeros, the feedback chain comprising IC_{2A}, IC_{2B}, IC_{2C}, and

R₅, C₂, IC_{1A}, AND NORMALLY OPEN MOMENTARY-CONTACT SWITCH S₁ CONSTITUTE A DEBOUNCED SWITCH THAT PROVIDES CLOCK PULSES FOR BOTH SECTIONS OF THE COUNTER.

IC_{4A} pulls Q₁'s base to a logic-high level, which in turn pulls one input of IC_{1B} to a logic low. This action causes the counter to skip the 00 state and advances the

count to the 01 state. Components R₅, C₂, IC_{1A}, and normally open momentary-contact switch S₁ constitute a debounced switch that provides clock pulses for both sections of the counter, IC₃. When a user pushes S₁, the counter advances to the 10 state, and a subsequent push advances the counter to the 11 state. A third push restarts the cycle. To summarize, IC_{4B} decodes the counter's 01 state and pulls CH₁ low, IC_{4C} decodes the counter's 10 state and pulls CH₂ low, and IC_{4D} decodes the counter's 11 state and pulls CH₃ low. The layout of the circuit should be non-critical, but use a low-leakage capacitor for C₁. Connect unused logic inputs to ground or V_{CC} as appropriate. **EDN**

Low-cost audio filter suppresses noise and hum

Richard M Kurzrok, RMK Consultants, Queens Village, NY

The low-cost composite passive filter in this Design Idea requires no dc power and can enhance the performance of audio equipment and instrumentation by rejecting power-supply hum and spurious pickup from AM, FM, and low-band VHF transmissions (Figure 1). The composite filter comprises a cascade of three simple filters: a T-section highpass filter to reject power-source hum and two π -section lowpass filters to reject spurious RF signals. As a starting point, the three filter sections present a lossless 0.01-dB Chebyshev response at a 50 Ω impedance level, but you can scale the components' values to meet other impedance requirements.

Table 1 lists the components the prototype filter uses. With the exception of inductor L₃, all the components are standard values that are available off the shelf. Switch S₁ provides a bypass mode that permits rapid frequency-response measurements without connection and disconnection of the prototype's BNC connectors. To construct

the prototype, wire all components to a section of perforated breadboard stock supported by metal spacers that mount inside a die-cast aluminum enclosure. This method of shielded construction has proved its worth in other laboratory-accessory applications (Reference 1). Table 2 lists the filter's measured insertion loss over a range of 40 Hz to 200 MHz.

Low-cost polarized electrolytic capacitors C₁ through C₆ provide rea-

sonable performance, but observe input polarity for signals with a dc component. For a modest increase in cost and assembly time, you can enhance filter performance and reproducibility by selecting the values of these capacitors to meet a 10% or better tolerance. For best results, use nonpolarized film-dielectric capacitors for C₁ through C₆. For noncritical applications, you can relax the tolerances for the remaining capacitors and use off-the-shelf inductors for 22-mH L₁, 0.68-mH L₂, and 3.9- μH L₃.

Redesigning the filter to match the 600 Ω impedance that you find in classic audio circuits would increase the

TABLE 1 COMPONENTS IN THE PROTOTYPE FILTER

Reference designators	Values	Description
C ₁ , C ₂ , C ₄ , C ₅	10 μF	50V electrolytic capacitor, $\pm 20\%$ tolerance
C ₃ , C ₆	4.7 μF	50V electrolytic capacitor, $\pm 20\%$ tolerance
C ₇ , C ₉	0.15 μF	Polypropylene capacitor, $\pm 2\%$ tolerance
C ₈ , C ₁₀	0.033 μF	Polypropylene capacitor, $\pm 2\%$ tolerance
C ₁₁ , C ₁₂	0.001 μF	Polypropylene capacitor, $\pm 2\%$ tolerance
L ₁	22 mH	Inductor, $\pm 5\%$ tolerance
L ₂	0.68 mH	Inductor, $\pm 10\%$ tolerance
L ₃	3.85 μH	Inductor, 27 turns of AWG #28 magnet wire hand-wound on T37-2 mixture (Carbonyl E) toroidal core
S ₁	NA	DPDT panel-mounted toggle switch
J ₁ , J ₂	NA	50 Ω BNC panel jack
NA	NA	Hammond 1590H-BK die-cast aluminum enclosure

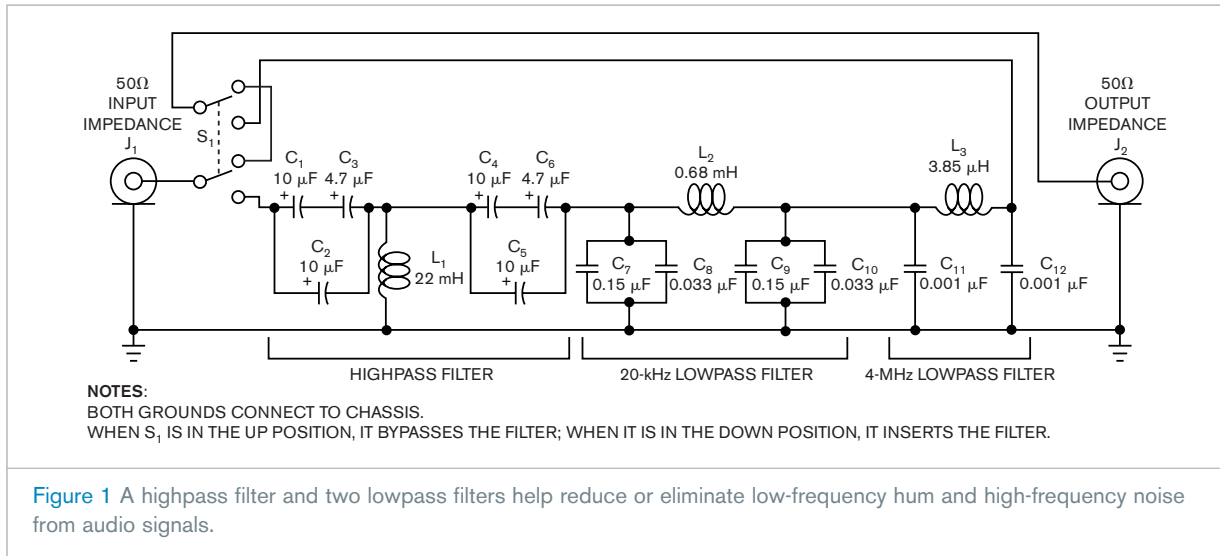


Figure 1 A highpass filter and two lowpass filters help reduce or eliminate low-frequency hum and high-frequency noise from audio signals.

inductors' values by an order of magnitude, which would increase the inductors' dimensions and costs. An alternative design approach could use cascaded active-RC filters, which would pave the way for their inclusion into completely integrated composite-audio filters. **EDN**

REFERENCE

1 Kurzrok, Richard M, "Simple Lab-Built Test Accessories for RF, IF, Baseband, and Audio," *High Frequency Electronics*, May 2003, pg 60.

TABLE 2 FILTER INSERTION LOSS

Frequency (kHz)	Insertion loss (dB)	Frequency (MHz)	Insertion loss (dB)
0.04	45.2	0.1	42.3
0.07	35.4	0.3	60
0.1	29.4	0.5	60
0.2	17.3	1	55.5
0.3	10.9	2	52.2
0.5	5.5	3	51.1
1	2.7	4	56.2
2	2	5	60
5	1.9	10	46.5
10	2.1	25	44
15	2.7	50	40.5
20	4.5	100	39.5
30	11.7	150	45
50	24.5	200	44

Microprocessor's single-interrupt input processes multiple external interrupts

Abel Raynus, Armatron International Inc, Malden, MA

On the lower end of the performance spectrum, many widely available and inexpensive microcontrollers pay for their small pc-board footprints by omitting functions. For example, most low-end processors provide only one external-interrupt input pin and only one address vector in memory for the service routine that processes external IRQs (interrupt requests). However, a

project occasionally requires that several interrupt-service programs must process multiple external interrupts from various sources. Cost and inventory constraints may make it undesirable to choose another microcontroller whose only advantage is the availability of a few more interrupt pins.

For example, Freescale Semiconductor's (www.freescale.com) popular

Nitron family of flash-memory microcontrollers, such as the MC68HC908QT and QY, offer only one IRQ input pin. You can use one-time-programmable versions of the family, such as the MC68HC705KJ1 or MC68HC705J1A, that offer five external-interrupt inputs but omit some of the family's valuable functions, such as flash memory, built-in analog-to-digital conversion, and an advanced instruction set. You could also select a larger microcontroller, such as the MC68HC908JL3, from the same product family to gain eight external-interrupt inputs at the expense of sig-

nificant increases in cost and pc-board area.

This Design Idea offers an alternative that retains the small processor and adds extra interrupt inputs. The technique involves applying the interrupt signals to an AND gate to generate an IRQ signal and using the microcontroller's inputs to recognize the interrupt's source. For example, consider the four external-interrupt sources in **Figure 1**. If you apply no interrupt signals and if all of the AND gate's inputs rest at logic ones, the IRQ level also remains at logic one. Applying an interrupt signal (a logic-zero level) to any one of four inputs, INT1 through INT4, drives the gate's output to a low level and triggers the interrupt. The interrupt-service routine recognizes the interrupt's source by testing the levels of input pins PA0, PA1, PA4, and PA5 and executing the corresponding interrupt-service routine.

The MC68HC908QY2 microcontroller, IC₁, includes built-in pullup

resistors that eliminate the need for external resistors, and you can use an inexpensive and readily available 74LS21 for IC₂. For demonstration purposes, this circuit displays the address of an incoming interrupt by lighting one of four corresponding LED indicators for 3 sec. The software routine in

Listing 1 that assigns a priority to each interrupt uses the standard set of assembler instructions and can apply to any microcontroller. You can download **Listing 1**, as well as the sample's assembler code and its accompanying table of equations (**Listing 2**), from www.edn.com/060302di1. **EDN**

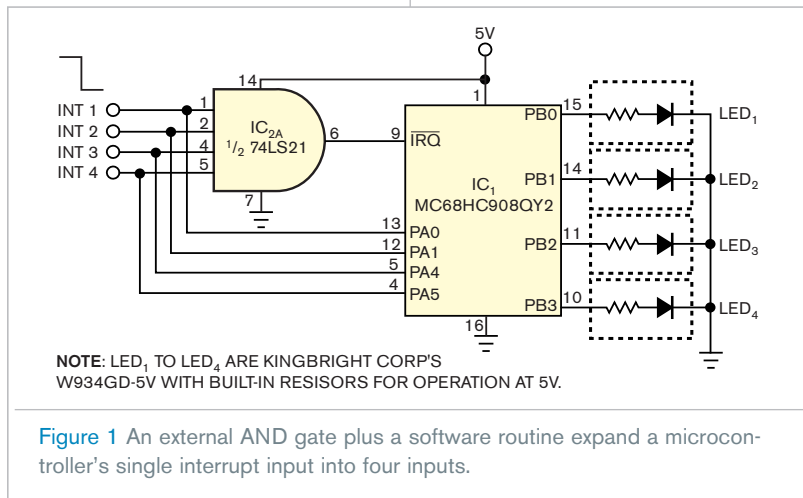


Figure 1 An external AND gate plus a software routine expand a microcontroller's single interrupt input into four inputs.