



$T=R \times C$, AND $F=1/(2 \times \pi \times T)$,
WHERE T IS THE TIME CONSTANT
IN SECONDS, AND F IS THE
CUTOFF -3-dB FREQUENCY.

Figure 1 In some circumstances,
a classic RC lowpass filter does
an adequate job of removing
noise from signals.