



Figure 1 A single 555 oscillator provides square-wave ac gate drive to an array of as many as 15 MOSFET-based solid-state relays.