



Figure 1 Connecting a low-dropout regulator's enable pin directly to the unregulated voltage input forces the output directly to the unregulated voltage input during the regulator's turn-on and turn-off intervals.