



**Figure 2** An alternative to directly connecting the regulator's input and enable pins, this "conventional" modification uses a resistor and a capacitor to delay the regulator's turn-on time. The diode eliminates the power-down delay interval.