



Figure 5 The addition of R_2 in Figure 3 solves the falling-edge problem, and shutdown occurs immediately after the input voltage drops too low. The regulator's output switches on only after sufficient voltage is present at its input.