



Figure 1 The isolated pulse driver transmits all duty cycles and consumes energy only during the gate charge and discharge processes.