



Figure 4 The top trace shows the driven transistor's gate-to-source voltage, and the bottom trace shows its collector-emitter voltage, which a probe attenuates. The transistor's load comprises a resistor that connects to a power supply.