



Figure 1 A pair of shift registers, an inverter, and a handful of precision resistors form a sine-wave generator (a). Two operational amplifiers form a resistance-capacitance lowpass filter that removes clock-signal artifacts from the output (b).