



Figure 2 A keypad matrix expands the CPLD circuit's control capabilities and retains the circuit's automatic power-off function.