



Figure 3 Adding the common-mode-reduction circuit in Figure 1 significantly reduces the amount of common-mode voltage on the video signal.