



Figure 1 This circuit drives a high-current, white LED at 93% efficiency over input voltage and temperature. Potentiometer R_1 controls current through LED_1 and allows brightness adjustment. Diode D_1 provides temperature compensation for LED_1 's forward-voltage drop.