



Figure 1 A pair of cascode-connected JFETs reduces the effects of power-supply-voltage fluctuations on a current source's accuracy.