



Figure 2 Setting  $R_1$  to values of  $1\text{ k}\Omega$ ,  $750\Omega$ , and  $510\Omega$  delivers output currents of approximately 1.8, 2.5, and 3.6 mA that are insensitive to a wide range of power-supply voltages.