



Figure 1 Use a pair of a PSOC microprocessor's internal blocks and a few external components to build a voltage-boost converter. Use a Schottky diode rated for a peak-inverse voltage of 100V for D₁. The PSOC's remaining pins are available for application support.