



Figure 2 A pulse-width modulator (top) and a comparator (bottom) can operate independently of other PSOC functions. Unconnected pins are available for additional functions.