



**Figure 1** This high-side constant-current source delivers load current of  $2.5\text{V}$  divided by the output resistance, provided that you choose the output resistance to ensure that the voltage between the regulator's input and ground terminals is at least  $2.5\text{V}$ .