



Figure 2 As in Figure 1, this low-side constant-current source draws a load current of 2.5V divided by the output resistance through the load resistance, provided that you select the output resistance to make the voltage difference between IC₁'s input and ground terminals at least 2.5V .