



Figure 3 If a capacitor short-circuits in the 5V-dc circuit of a pc-board assembly, the voltage is safe, and the current is only 0.5 mA during normal operation.

---