



Figure 1 A classic generalized impedance converter provides a single-port impedance that appears at V_{IN} . The schematic omits power connections for clarity.