



Figure 2 Replacing all of a GIC's impedances with resistors creates a constant-current source.