



Figure 1 A zener diode, two stages of amplification, and an FM voltage-controlled oscillator form a constant-amplitude dither generator.