



Figure 1 This simple circuit requires only a single IC to balance the charges on two series-connected, low-voltage, high-value capacitors and maintain their common junction at one-half of the supply voltage.