



Figure 4 Adding Q<sub>3</sub>, Q<sub>4</sub>, and the bootstrapped negative-bias generator comprising D<sub>2</sub>, D<sub>3</sub>, and C<sub>4</sub> reduces the circuit's quiescent current from 25 mA to 1 mA.